 





VGA Driver

Nikolaos Karapoulatidis, Shehroz Bashir Malik, Christian Stratmann


VGA Signals



Concept Design

 

Block Diagram

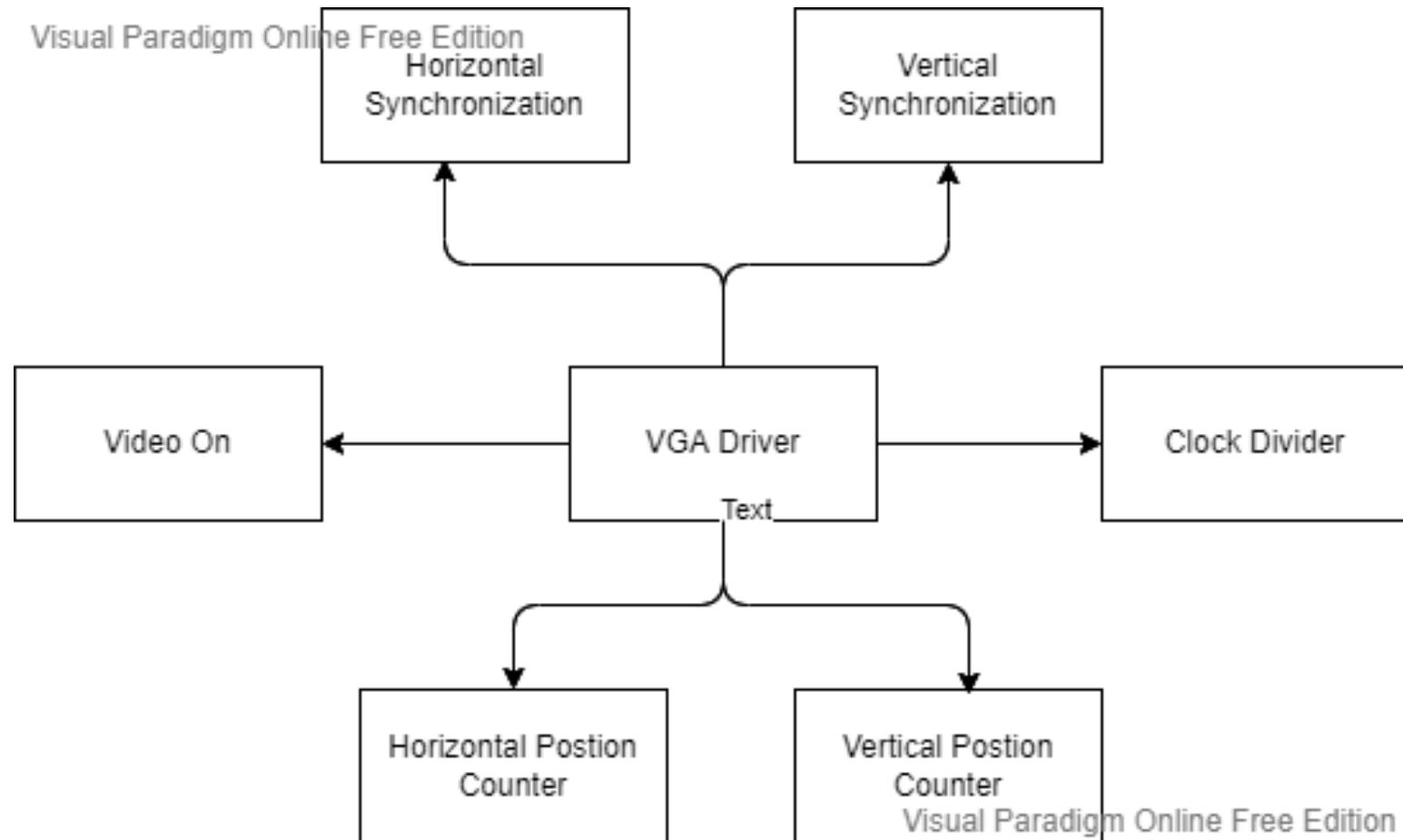

Entity

- **Input:** Clock and reset with type STD_logic
- **Output:** Horizontal Sync and Vertical Sync with type STD_logic, Red Green Blue with STD_Logic_Vector

Architecture

- **Signals:** Clock25, Horizontal Position, Vertical Position and VideoOn
- **Constants for Horizontal** (pixel number): Display, front porch, back porch, sync pulse/retrace
- **Constants for Vertical** (line number): Display, upper porch, lower porch, sync pulse/retrace

Processes I

- Every **process depends on the rising edge** of the clock
- **Clock Divider:** creates a clock of 25 mHz (default is 50mHz)
- **Horizontal Position Counter:** horizontal position = the total horizontal pixels? If true then start from left side, if not then counter++ and head to the next pixel
- **Vertical Position Counter:** If true when start from the top

Processes II

- **Horizontal Synchronization:** checks if the actual horizontal position is inside the horizontal front porch or back porch. If true then HSYNC set to 1
- **Vertical Synchronization:** checks for upper and lower porch
- **Video On Check:** ensures that the video is only on when the actual position is not inside a porch

Processes III

- **Draw Box:** set the output RGB to 111 if we are between 10 and 60 for the horizontal position and vertical position, outside those boundaries RGB is set to 000
-> white square appears on the VGA monitor


Testbench

- testbench is toggling the clock every 5ns and the reset every 100ns




RTL Schematic I


```
1 NET "CLK" LOC = "C9" | IOSTANDARD = LVCMOS33 ;
2 NET "RST" LOC = "P14" ;
3
4 NET "RGB<0>" LOC = "H14" | IOSTANDARD = LVTTTL | DRIVE = 8 | SLEW = FAST ;
5 NET "RGB<1>" LOC = "H15" | IOSTANDARD = LVTTTL | DRIVE = 8 | SLEW = FAST ;
6 NET "RGB<2>" LOC = "G15" | IOSTANDARD = LVTTTL | DRIVE = 8 | SLEW = FAST ;
7 NET "HSYNC" LOC = "F15" | IOSTANDARD = LVTTTL | DRIVE = 8 | SLEW = FAST ;
8 NET "VSYNC" LOC = "F14" | IOSTANDARD = LVTTTL | DRIVE = 8 | SLEW = FAST ;
9
```

 

RTL Schematic II

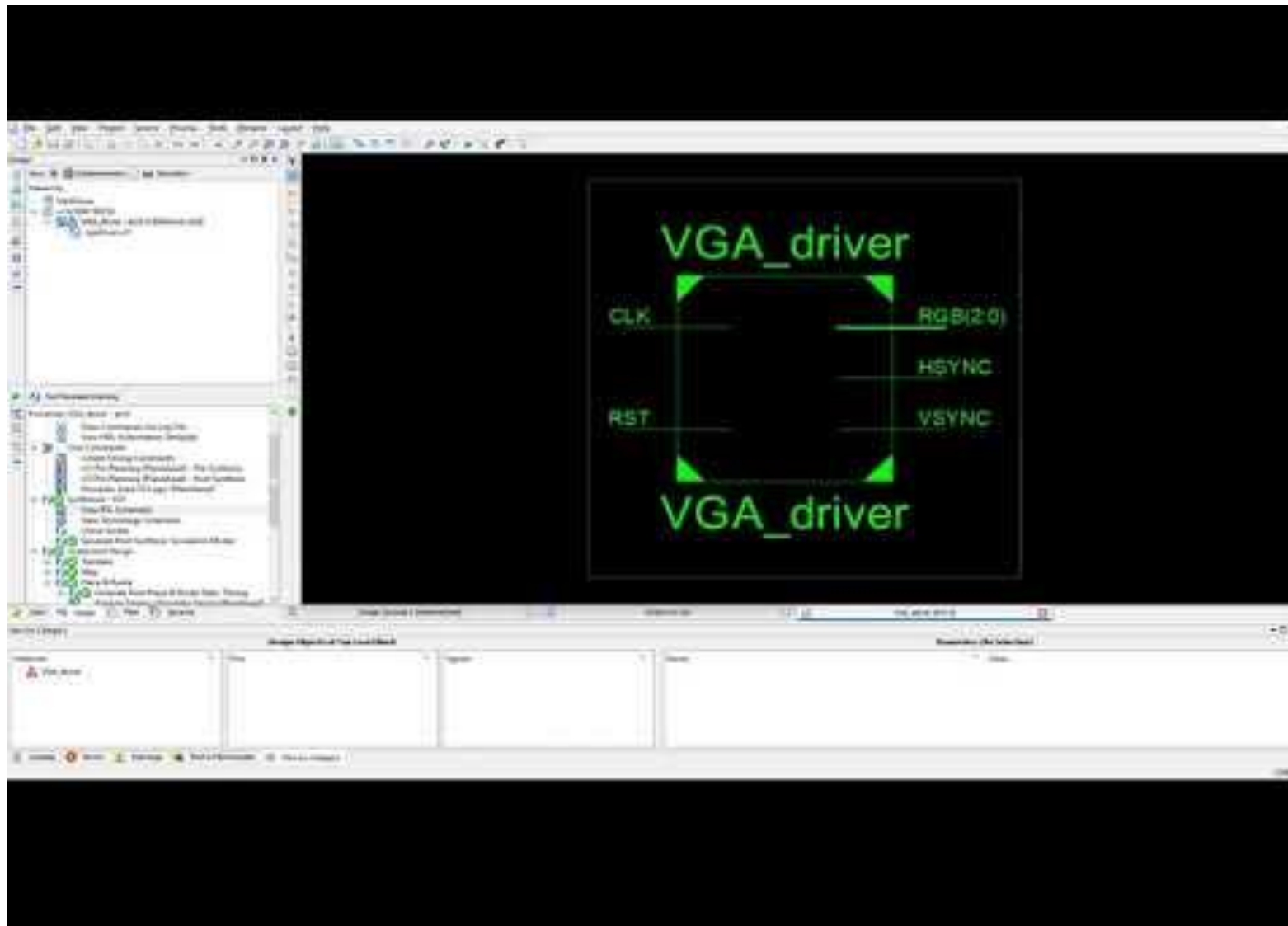


Routed Design

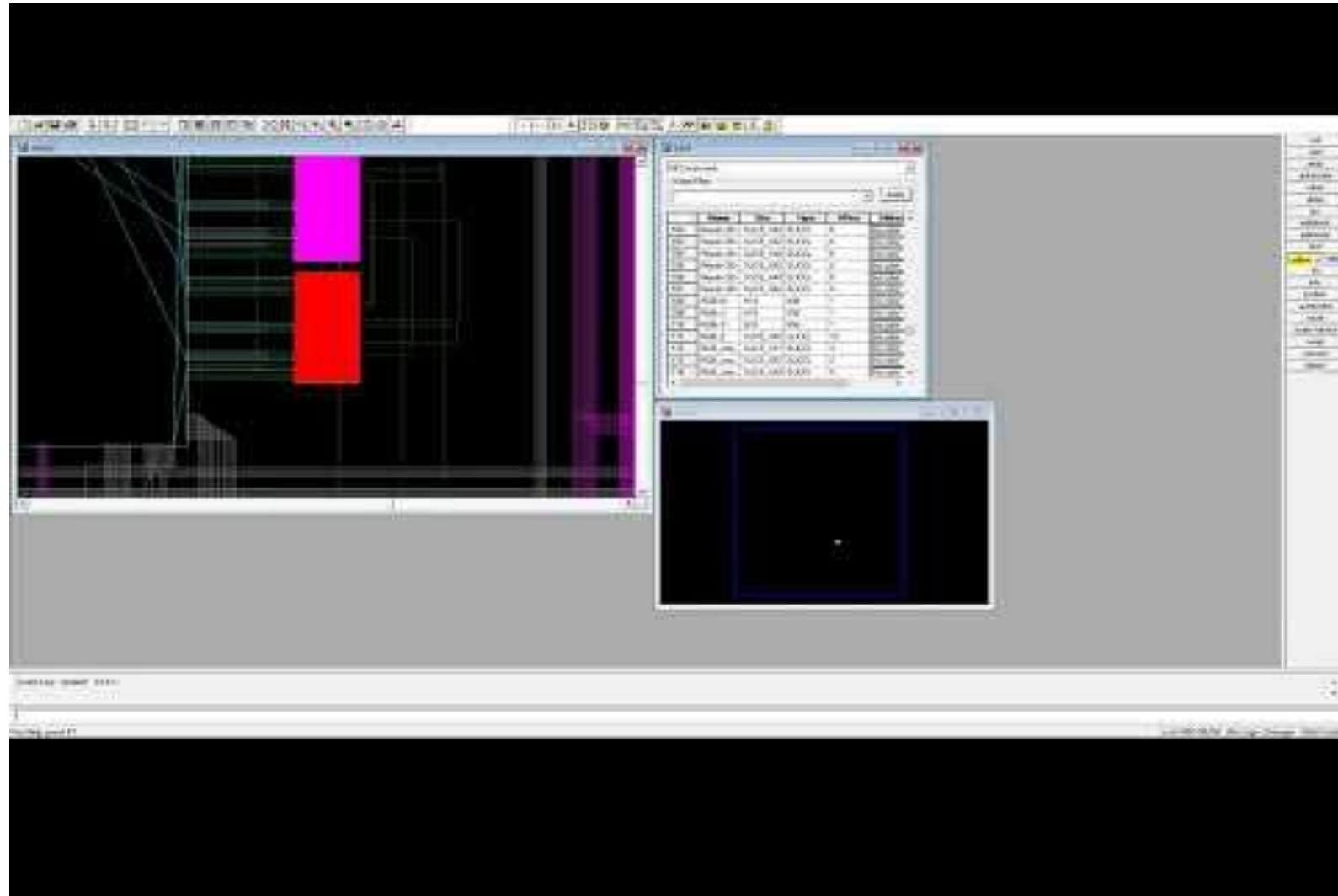

PCB schematic

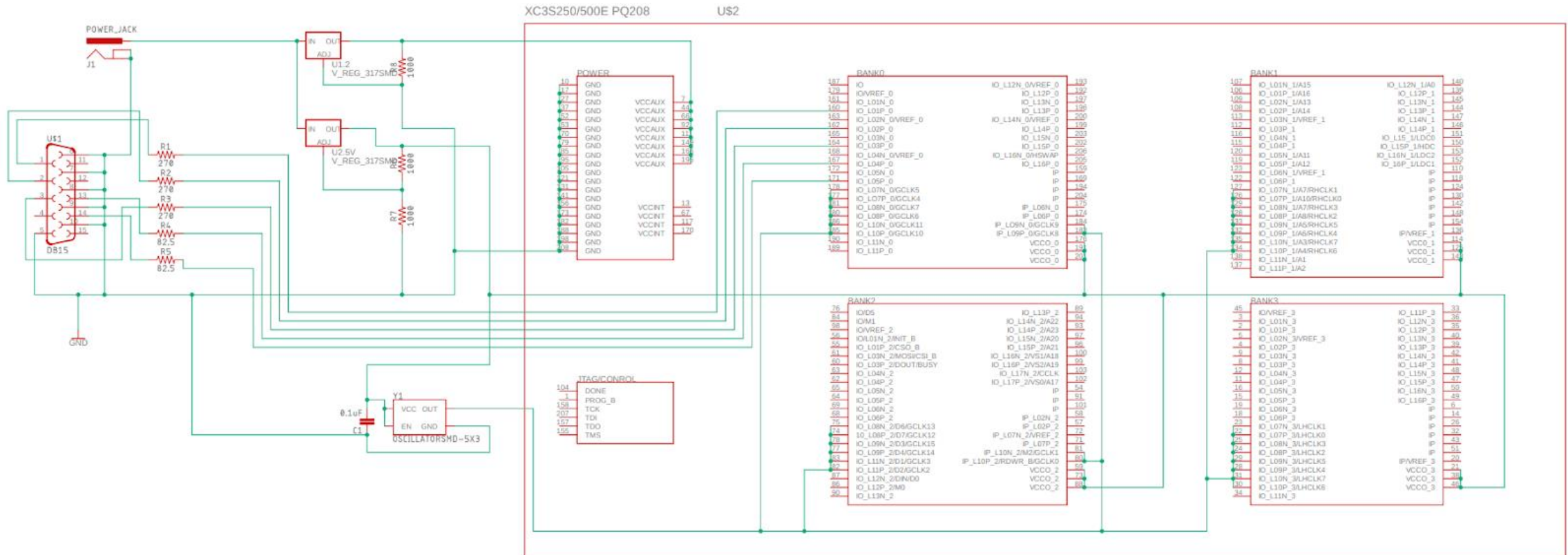- Spartan 3E from Xilinx
- Two 317 voltage regulators (2.5 and 1.2 volts)
- Oscillator is providing a 25 MHz clock signal




PCB layout

- Width: 80.1 mm
- Length: 67.5 mm

| Part | Value | Package | Cost |
|-------|----------|---------|-------------------|
| C1 | 0.1 uF | 0603 | 0.10€ |
| J1 | PW_Jack | | 0.62€ |
| R1-3 | 270 Ohm | 0603 | 0.55€ (10 pieces) |
| R4-5 | 82.5 Ohm | 0603 | 0.50€ (5 pieces) |
| R6-8 | 1000 Ohm | 0603 | 0.45€ (10 pieces) |
| U\$2 | | | 22.07€ |
| V_REG | 317SMD | SOT223 | 1.30€ (2 pieces) |
| Y1 | | | 1.68€ |

Total cost for the components: €27.27

PCB: ~€4.74 (with shipping ~€25)

 

Conclusion

VGA Concepts examined

Succesfully implemented in VHDL

PCB Schematic explored

Ready for FPGA Implementation